

**CERTIFICATES OF COMPETENCY IN THE MERCHANT NAVY –  
MARINE ENGINEER OFFICER**

EXAMINATIONS ADMINISTERED BY THE  
**SCOTTISH QUALIFICATIONS AUTHORITY**  
ON BEHALF OF THE  
**MARITIME AND COASTGUARD AGENCY**

**STCW 95 CHIEF ENGINEER REG. III/2 (UNLIMITED)**

**041-33 - ELECTROTECHNOLOGY**

**THURSDAY, 18 OCTOBER 2012**

**0915 - 1215 hrs**

Examination paper inserts:

Worksheet Q3

Notes for the guidance of candidates:

1. Non-programmable calculators may be used.
2. All formulae used must be stated and the method of working and ALL intermediate steps must be made clear in the answer.

Materials to be supplied by examination centres:

Candidate's examination workbook  
Graph Paper



**ELECTROTECHNOLOGY**

**Attempt SIX questions only.**

**All questions carry equal marks.**

**Marks for each part question are shown in brackets.**

1. For the network shown in Fig Q1 calculate EACH of the following:

- (a) the current in the indicating meter. (8)
- (b) the value to which the 1 kΩ resistor must be changed to make the current in the meter 1mA in the direction found in Q1(a). (8)

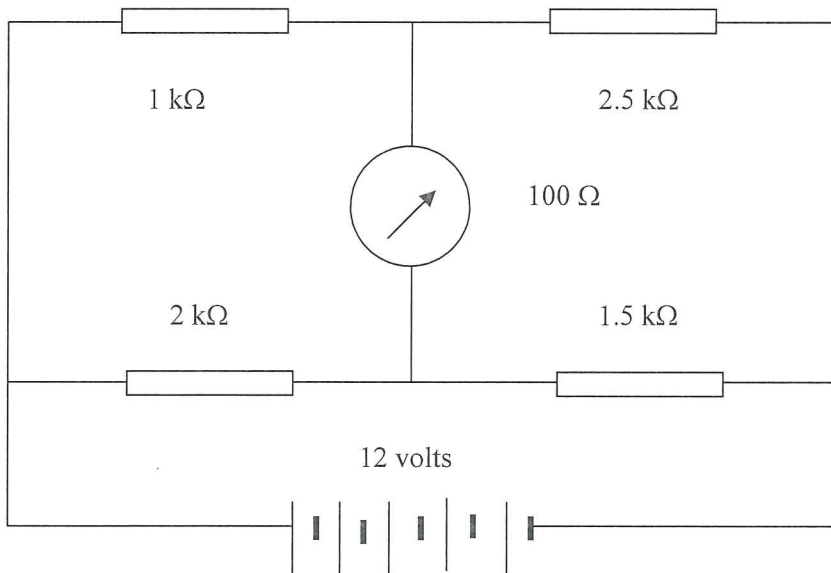


Fig Q1

2. A circuit comprises a resistor of 800 Ω in series with a non-linear element whose characteristic is given by  $I = 0.5V^{3/2}$  where I is in mA and V is in volts. The circuit is connected to a 12 V d.c. supply.

Determine EACH of the following:

- (a) the circuit current; (6)
- (b) the voltage across the non-linear element; (4)
- (c) the value to which the 800 Ω resistor must be changed to make the circuit current 10 mA. (6)

3. A power silicon transistor with the characteristics given in Worksheet Q3 is operated from a 16 V d.c. supply. The operating ('quiescent') point is  $I_b = 40 \text{ mA}$  and  $I_c = 2 \text{ A}$ .

Determine EACH of the following:

- (a) draw the load line on the characteristics; (4)
- (b) (i) the value of the collector load resistance; (4)
- (ii) the peak-to-peak variation in collector current if a signal of  $\pm 20 \text{ mA}$  is applied to the base; (2)
- (iii) the corresponding variation in collector current; (2)
- (iv) the power dissipated in the transistor due to this signal. (4)

4. An a.c. series circuit consists of four elements as shown in Fig Q4. The power dissipated in the  $50 \Omega$  resistor is  $200 \text{ W}$  and the volt drops across the various parts of the circuit are as shown.

Calculate EACH of the following:

- (a) the values of C and L; (8)
- (b) the overall power factor of the circuit; (5)
- (c) the kVAr for the inductance. (3)

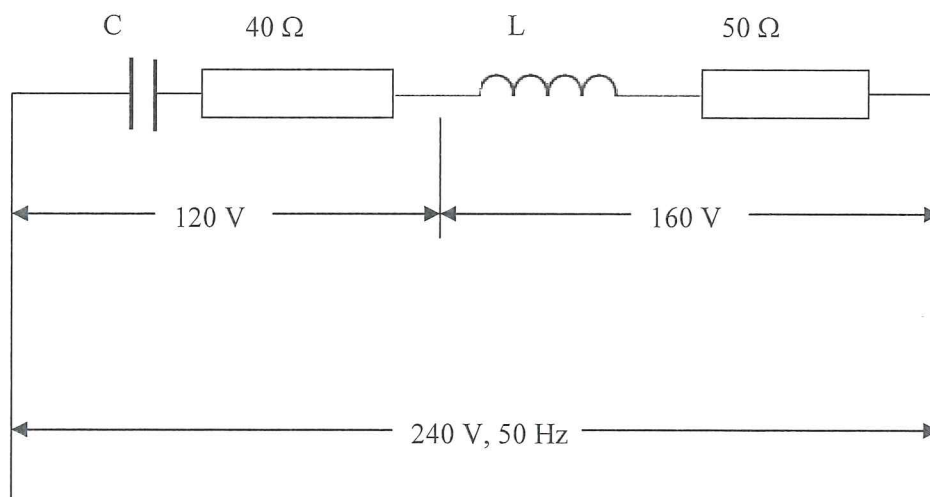


Fig Q4

5. A three phase star connected load each phase of which consists of a coil of resistance  $40 \Omega$  and inductance  $0.1 \text{ H}$  is connected together with a delta connected load, each phase of which comprises a resistor of  $120 \Omega$  in series with a  $70 \mu\text{F}$  capacitor, to a supply of  $440 \text{ V}$   $50 \text{ Hz}$ .

Calculate EACH of the following:

- (a) the line current for each load; (6)
- (b) the total line current drawn from the supply; (6)
- (c) the overall power factor for the two loads. (4)

6. A  $440 \text{ V}/110 \text{ V}$  single phase transformer is rated at  $40 \text{ kVA}$  full load output. The iron loss is  $3 \text{ kW}$  and it operates at maximum efficiency when delivering  $80\%$  full load.

Calculate EACH of the following:

- (a) the full load copper loss; (5)
- (b) the full load efficiency at  $0.9$  power factor; (5)
- (c) the efficiency at  $80\%$  full load and unity power factor. (6)

7. With reference to a double cage induction motor:

- (a) sketch a cross section through part of the rotor; (4)
- (b) explain the operation of the motor from start up to operating speed; (8)
- (c) sketch a torque speed curve for each cage on the same pair of axes. (4)

8. (a) Explain the operating principle of a double wound single phase power transformer. (5)
- (b) State why the transformer is rated in  $\text{kVA}$  rather than  $\text{kW}$ . (3)
- (c) Explain why the transformer will overheat if operated at a frequency less than the designed frequency. (5)
- (d) State the relationship between iron losses and copper losses for maximum efficiency. (3)

9. (a) Explain what is meant by the expression *single phasing*. (6)
- (b) Explain the probable effect of single phasing on a squirrel cage motor operating on load. (4)
- (c) State ONE method by which a motor can be protected against the effects of single phasing. (6)

(This Worksheet must be returned with your answer book)

# COMMON EMITTER TRANSISTOR CHARACTERISTICS

TYPE	SCALE FACTORS per unit value of	
	$I_b$	$I_c$
1. Small Si	1 $\mu$ A	1 mA
2. Power Si	1 mA	1 A

