

**CERTIFICATES OF COMPETENCY IN THE MERCHANT NAVY -
MARINE ENGINEER OFFICER**

EXAMINATIONS ADMINISTERED BY THE
SCOTTISH QUALIFICATIONS AUTHORITY
ON BEHALF OF THE
MARITIME AND COASTGUARD AGENCY

STCW 78 as amended MANAGEMENT ENGINEER REG. III/2 (UNLIMITED)

040-33 - ELECTROTECHNOLOGY

THURSDAY, 19 OCTOBER 2017

0915 - 1215 hrs

Examination paper inserts:

--

Notes for the guidance of candidates:

- | |
|---|
| <ol style="list-style-type: none">1. Non-programmable calculators may be used.2. All formulae used must be stated and the method of working and ALL intermediate steps must be made clear in the answer. |
|---|

Materials to be supplied by examination centres:

Candidate's examination workbook Graph paper

ELECTROTECHNOLOGY

Attempt SIX questions only.

All questions carry equal marks.

Marks for each part question are shown in brackets.

1. A 525 m, two core distributor cable is fed at one end with 240 V d.c. and at the other end with 250 V d.c.

The following loads are applied at distances measured from 240 V end:

- Load 1 10 A at 100 m
- Load 2 100 A at 250 m
- Load 3 70 A at 450 m
- Load 4 25 A at 500 m

The cable resistance (go and return) is 0.08Ω per 100 m.

Calculate EACH of the following:

- (a) the current supplied at each end of the cable distributor; (6)
- (b) the voltage at each load point; (8)
- (c) the power delivered at each end of the cable distributor. (2)
2. A relay coil has a resistance of 200Ω and the current required to operate the relay is 150 mA.
- When the coil is connected to a 50 V d.c. it takes 40 ms for the relay to operate.
- (a) Calculate EACH of the following:
- (i) the steady state relay current; (2)
- (ii) the time constant for the coil; (4)
- (iii) the inductance of the coil. (4)
- (b) To increase the operating time for the relay, a 50Ω resistor is connected in series with the coil.
- Determine the new operating time for the relay. (6)

3. A star connected three phase load has a coil of resistance 50Ω and inductance 0.1 H in each phase. The load is connected to a three phase, 440 V , 60 Hz supply.

Calculate EACH of the following:

- (a) the line current; (5)
- (b) the power factor of the load; (4)
- (c) the value of each of three identical delta connected capacitors which if connected in parallel with this load will raise the overall power factor to unity. (7)
4. A three phase, four pole induction motor runs on a 440 V , 50 Hz supply. It delivers a shaft output power of 50 kW . The rotational losses (windage and friction) amount to 4 kW and the speed is 24 rev/s .

If the input current is 120 A at a lagging power factor of 0.7 and the stator copper loss is 3 kW , calculate EACH of the following:

- (a) the rotor copper loss; (6)
- (b) the stator iron loss; (6)
- (c) the efficiency. (4)
5. Two, six pole, three phase a.c. generators operating in parallel supply a total load of 2000 kVA at a power factor of 0.8 lagging.

Their load characteristics are linear with the test results given in Table Q5.

Generator	Speed/kW	Voltage/kVAR
No. 1	1440 rev/min on No-load 1200 rev/min on 1200 kW	500 V on No-load 415 V on 1000 kVAR
No. 2	1360 rev/min on No-load 1180 rev/min on 900 kW	490 V on No-load 425 V on 800 kVAR

Table Q5

Determine EACH of the following:

- (a) the supply frequency; (6)
- (b) the bus-bar voltage; (6)
- (c) the kVA output of each generator; (2)
- (d) the operating power factor of each generator. (2)

6. A 60 kVA, 440 V/110 V single phase transformer has iron loss of 4 kW, and a full load copper loss of 6 kW.

Calculate EACH of the following:

- (a) the kVA output at which maximum efficiency will be achieved; (8)
- (b) the efficiency at 50 kW output and 0.85 power factor. (8)
7. (a) Explain the meaning of the term *power factor*. (3)
- (b) State TWO advantages of power factor correction. (4)
- (c) Explain, with the aid of a circuit diagram, how power factor correction can be achieved in a three phase circuit using capacitors. (5)
- (d) Explain ONE method other than the use of capacitors by means of which power factor correction may be achieved. (4)
8. With reference to a three phase brushless generator system:
- (a) sketch a labelled diagram showing the essential features; (7)
- (b) describe the system sketched in Q8(a); (7)
- (c) state ONE advantage and ONE disadvantage. (2)
9. A single phase, 230 V, 50 Hz, 3:1 transformer has a secondary winding resistance of 1Ω and supplies a half wave rectifier circuit. The rectifier circuit has a resistive load of 680Ω and the diode has a forward resistance of 14Ω .
- (a) Sketch EACH of the following:
- (i) a labelled circuit diagram; (3)
- (ii) the load voltage waveform indicating maximum and average voltage levels. (3)
- (b) Calculate EACH of the following load values:
- (i) the maximum current; (5)
- (ii) the average current; (3)
- (iii) the average voltage. (2)