

## ELECTRO TECHNOLOGY\_ JULY 2019

1. A 2000 m, 2-core cable is used as a ring main feeder supplied at both ends with 220 V d.c. Loads of 100 A, 150 A, 200 A, and 50 A are connected at points 500 m, 800 m, 1200 m, and 1700 m measured respectively from one end.

The cable resistance (go + return) is  $0.2 \Omega/\text{km}$ .

- (a) Calculate the current in each cable section. (10)
- (b) Show the current direction on a one-line sketch of the ring main. (2)
- (c) Calculate the p.d. at each load point. (4)

2. A relay coil has a resistance of  $400 \Omega$  and the current required to operate the relay is 45 mA.

When the coil is connected to a 24 V d.c. supply it takes 30 ms for the relay to operate.

- (a) Calculate EACH of the following:
- (i) the steady-state relay current; (2)
- (ii) the time constant for the coil; (4)
- (iii) the inductance of the coil. (4)
- (b) To increase the operating time for the relay, a  $40 \Omega$  resistor is connected in series with the coil.

Determine the new operating time for the relay. (6)

## ELECTRO TECHNOLOGY\_ JULY 2019

---

3. (a) Three identical coils of impedance  $Z$  are to be connected to a balanced three-phase a.c. power supply of line voltage  $V_L$ . When the coils are star connected, the line currents are one third of the line currents when delta connected.

Using relationships for balanced three-phase circuits, show that this ratio is correct. (4)

- (b) Three identical coils connected in delta across a three-phase, 415 V, 50 Hz power supply have a total power demand of 12 kW with line current of 25 A.

(i) Calculate the supply power factor. (2)

(ii) Determine the resistance and inductance of each coil. (6)

- (c) The supply frequency is now raised to 60 Hz while the voltage remains constant.

Calculate the new line current and the total power supplied. (4)

4. A three-phase, eight-pole induction motor runs on a 440 V, 60 Hz supply. It delivers a shaft output power of 7 kW at a speed of 14.4 rev/s and operates at a power factor of 0.8 lagging. The stator and rotational (windage + friction) losses amount to 0.6 kW and 0.4 kW respectively.

Calculate EACH of the following:

(a) the slip; (3)

(b) the frequency of the rotor e.m.f; (2)

(c) the input power to the motor; (8)

(d) the motor line current. (3)

## ELECTRO TECHNOLOGY\_ JULY 2019

---

5. A three-phase, 440 V, 60 Hz shaft-generator supplies the following loads:
- incandescent lighting and heating 80 kW at unity pf
  - fluorescent lighting 60 kW at 0.9 pf lagging
  - navigation aids and miscellaneous 45 A at 0.85 pf lagging
  - induction motors 240 kW at 0.8 pf lagging
- (a) Determine the total kW, kVAr, kVA and the overall power factor of the ship's load. (10)
- (b) A three-phase synchronous motor which takes 70 kW is now connected to the power system.
- Determine EACH of the following:
- (i) the required power factor of this motor to cause the shaft generator to operate at unity power factor; (3)
- (ii) the current taken by the synchronous motor. (3)

6. (a) With reference to an autotransformer:
- (i) sketch a labelled diagram; (3)
- (ii) describe how this autotransformer is different to an ordinary power transformer; (2)
- (iii) state FOUR advantages compared to an ordinary power transformer; (4)
- (iv) state ONE shipboard application of an autotransformer. (1)
- (b) An autotransformer is used to supply a single-phase, 230 V, 2 kW, unity power factor load from a 400 V supply.
- Calculate EACH of the following, neglecting the losses:
- (i) the current in the turns connected across the load; (3)
- (ii) the current in the turns not connected across the load. (3)

## ELECTRO TECHNOLOGY\_ JULY 2019

---

7. (a) Sketch and label the V/I characteristics of a three-phase generator operating at constant speed with EACH of the following load power factors:
- (i) unity; (2)
  - (ii) 0.8 lagging; (2)
  - (iii) 0.8 leading. (2)
- (b) Explain why it is recommended that two identical a.c. generators running in parallel should operate at similar power factors. (5)
- (c) Explain how the power factor of paralalled a.c. generators may be altered independently of the ship's load power factor. (5)
8. (a) Explain, with the aid of a labelled power triangle, the term *power factor*. (6)
- (b) State TWO reasons why low power factor is undesirable. (2)
- (c) Explain how power factor correction can be achieved in a three-phase circuit using capacitors. (4)
- (d) Explain how a synchronous motor may assist in power factor correction. (4)
9. A single-phase, 3:1 step-down transformer has a primary voltage of 230 V and supplies a half-wave rectifier circuit. The transformer has a secondary winding resistance of  $1\ \Omega$ . The rectifier circuit has a resistive load of  $680\ \Omega$  and the diode has a forward resistance of  $14\ \Omega$ .
- (a) Sketch EACH of the following:
- (i) a labelled circuit diagram; (3)
  - (ii) the load voltage waveform indicating maximum and average voltage levels. (3)
- (b) Calculate EACH of the following load values:
- (i) the maximum current; (4)
  - (ii) the average current; (3)
  - (iii) the average voltage. (3)