

**CERTIFICATES OF COMPETENCY IN THE MERCHANT NAVY -
MARINE ENGINEER OFFICER**

STCW 78 as amended MANAGEMENT ENGINEER REG. III/2 (UNLIMITED)

040-33 - ELECTROTECHNOLOGY

THURSDAY, 21 JULY 2022

0915 - 1215 hrs

Materials to be supplied by examination centres

Candidate's examination workbook
Graph paper

Examination Paper Inserts

1. Examinations administered by the SQA on behalf of the Maritime & Coastguard Agency.
2. Candidates should note that 96 marks are allocated to this paper. To pass, candidates must achieve 48 marks.
3. Non-programmable calculators may be used.
4. All formulae used must be stated and the method of working and all intermediate steps must be made clear in the answer.



ELECTROTECHNOLOGY

Attempt SIX questions only.

All questions carry equal marks.

Marks for each part question are shown in brackets.

1. Fig Q1 shows a ring main of total length 1000 m and resistance (go + return) of $0.002 \Omega/\text{m}$. The ring main is supplied with 240 V d.c. and the following loads are connected to the ring at distances measured clockwise from the supply point:

- 60 A at 200 m
- 90 A at 500 m
- 150 A at 700 m

Calculate EACH of the following:

- (a) the currents in sections AB and AD; (6)
- (b) the lowest voltage across any of the three loads; (5)
- (c) the total power loss in the ring main. (5)

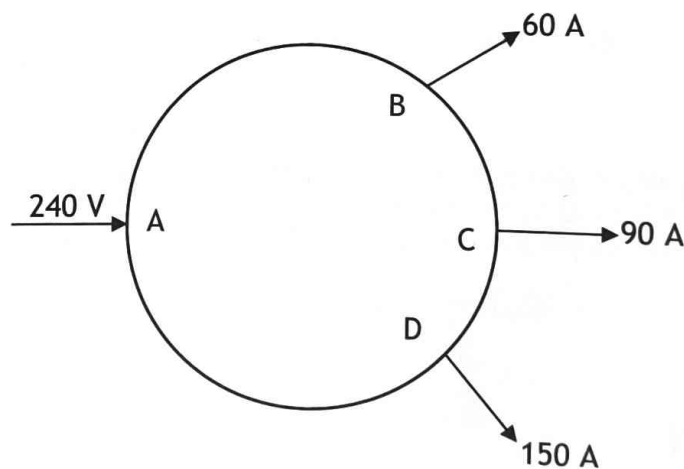


Fig Q1

2. A relay has a time constant of 5 ms and starts to operate 0.52 ms after connection to a 20 V d.c. supply.
- (a) If the instantaneous current is 200 mA, calculate EACH of the following:
- (i) the final steady state relay current; (6)
 - (ii) the resistance and inductance of the relay coil. (4)
- (b) To increase the operating time a $40\ \Omega$ resistor is connected in series with the relay coil.
- Calculate the new operating time for the relay assuming the instantaneous current is 200 mA. (6)
3. A balanced, three-phase, star connected load of 200 kW takes a leading current of 160 A from a 1.1 kV, 60 Hz supply.
- Calculate EACH of the following:
- (a) the resistance per phase; (6)
 - (b) the capacitance per phase; (3)
 - (c) the power factor; (2)
 - (d) the power consumed if the same load is connected in delta. (5)
4. A three-phase, 440 V, 60 Hz, 6 pole induction motor runs at a power factor of 0.82 lag and drives a load of 11 kW at a speed of 19.6 rev/s. The stator loss is 1.3 kW and the rotational losses (windage and friction) amount to 1.0 kW.
- Calculate EACH of the following:
- (a) the synchronous speed; (3)
 - (b) the rotor copper loss; (6)
 - (c) the input power to the motor; (4)
 - (d) the motor current. (3)

5. A three-phase, 440 V, 60 Hz shaft-generator supplies the following loads:
- incandescent lighting and heating 80 kW at unity pf
 - fluorescent lighting 60 kW at 0.9 pf lagging
 - navigation aids and miscellaneous 45 A at 0.85 pf lagging
 - induction motors 240 kW at 0.8 pf lagging
- (a) Determine the total kW, kVAr, kVA and the overall power factor of the ship's load. (10)
- (b) A three-phase synchronous motor which takes 70 kW is now connected to the power system.
- Determine EACH of the following:
- (i) the required power factor of this motor to cause the shaft generator to operate at unity power factor; (3)
- (ii) the current taken by the synchronous motor. (3)
6. A 250 kVA single-phase transformer has iron losses of 1.8 kW. The full load copper loss is 2 kW.
- Calculate EACH of the following:
- (a) efficiency at full load, 0.8 lagging p.f.; (6)
- (b) kVA supplied at maximum efficiency; (4)
- (c) maximum efficiency at 0.7 lagging p.f. (6)
7. With reference to shipboard electrical distribution systems:
- (a) describe the meaning of the term *earth fault*; (2)
- (b) explain the term *earth bonding* of electrical equipment, stating how it is achieved; (3)
- (c) sketch a circuit diagram of one arrangement for detecting phase to earth faults in a shipboard high voltage three-phase system; (6)
- (d) calculate the value of a neutral earthing resistor (NER) to limit the earth fault current to the full load rating of a 2 MW, 0.8 p.f., 3.3 kV, three-phase neutral earthed a.c. generator. (5)

8. (a) With reference to the principle of operation of a synchronous motor, explain how it differs from that of an induction motor. (4)
- (b) Explain why a synchronous motor is unable to produce starting torque. (6)
- (c) State how an electronic converter is used to start a synchronous motor. (3)
- (d) State THREE shipboard applications of synchronous motors. (3)
9. With reference to a single-phase, full-wave bridge rectifier:
- (a) sketch a labelled circuit diagram; (4)
- (b) explain the circuit operation; (4)
- (c) sketch labelled waveforms to show the relationships between EACH of the following:
- (i) the bridge input voltage; (2)
- (ii) the current through each diode; (4)
- (iii) the load current. (2)