

ELECTROTECHNOLOGY

Attempt SIX questions only.

All questions carry equal marks.

Marks for each part question are shown in brackets

1. A 110 V battery with internal resistance of 0.3Ω , is connected in parallel with a 120 V d.c. generator with internal resistance 0.5Ω . This parallel combination supplies a 5Ω load.
 - (a) Sketch a labelled circuit diagram. (3)
 - (b) Calculate EACH of the following:
 - (i) the battery current; (8)
 - (ii) the load current. (4)
 - (c) State whether the battery is charging or discharging. (1)

2. (a) A $33 \mu\text{F}$ capacitor is charged from a 100 V d.c. supply via a $47 \text{ k}\Omega$ resistor for 3 seconds. This capacitor is then disconnected from the supply and a $68 \mu\text{F}$ capacitor is charged from the same supply via the same resistor for 5 seconds.

Calculate EACH of the following:

 - (i) the voltage to which each capacitor has charged; (8)
 - (ii) the charge stored in each capacitor. (3)
- (b) The charged capacitors in Q2(a) are connected in parallel.

Calculate the final voltage across the parallel circuit. (5)

3. An unbalanced, three-phase, star connected load is supplied from a four-wire, 440 V, 50 Hz supply. The current in EACH phase is:
- $I_R = 7$ A lagging V_R by 30°
 - $I_S = 5$ A in phase with V_S
 - $I_T = 9$ A leading V_T by 60°
- (a) Sketch, approximately to scale, a labelled phasor diagram showing phase voltages and currents. (3)
- (b) Calculate EACH of the following:
- (i) the neutral current; (5)
 - (ii) the phase angle of the neutral current with respect to the S phase voltage; (2)
 - (iii) the total power dissipated. (6)
4. (a) With reference to a three-phase synchronous motor:
- (i) explain why the motor is not self-starting; (3)
 - (ii) describe ONE starting method; (2)
 - (iii) describe how the motor responds to increasing load if the excitation is constant; (3)
 - (iv) state the effect on motor power factor if the excitation is reduced. (1)
- (b) A 50 kW synchronous motor operates at full-load with an efficiency of 90% and power factor 0.92 lead.
- Calculate EACH of the following motor input values:
- (i) active power (kW); (2)
 - (ii) reactive power (kVAr); (3)
 - (iii) apparent power (kVA). (2)

5. Two, three-phase, four-pole generators operate in parallel and share a 3200 kVA load with a power factor of 0.75 lag. Both generators have linear characteristics with test results as shown in Table Q5.

GENERATOR	SPEED/kW	VOLTAGE/kVAr
G1	1900 rev/min at no-load	460 V at no-load
	1825 rev/min at 900 kW	450 V at 400 kVAr
G2	1875 rev/min at no-load	455 V at no-load
	1850 rev/min at 400 kW	446 V at 1000 kVAr

Table Q5

Determine EACH of the following:

- (a) the busbar frequency; (7)
- (b) the busbar voltage; (6)
- (c) the power factor of EACH generator. (3)
6. (a) Sketch a labelled circuit diagram for a 440V, step-down, star connected, three-phase autotransformer with 50%, 65% and 80% tapings. Indicate primary and secondary phase turns, voltages and currents. (5)
- (b) State TWO advantages and the main disadvantage of an autotransformer compared to a double wound transformer. (3)
- (c) A three-phase, 440 V induction motor having a full-load current of 75 A is connected to the 65% tapings of the autotransformer in Q6(a). The motor starting current is 6 x full-load when started D.O.L.

Calculate EACH of the following at start:

- (i) the current in each section of the transformer phases; (4)
- (ii) the voltage across each section of the transformer phases; (3)
- (iii) the motor line voltage. (1)

7. (a) With the aid of a labelled cross-sectional sketch, describe the construction of a four pole salient rotor for a synchronous generator. (6)
- (b) A three-phase, star connected, 500 kVA, 440 V generator has negligible stator winding resistance and synchronous reactance of $0.2 \Omega/\text{phase}$. The generator load demands full-load current at 0.8 power factor lag. (4)
- (i) Sketch a labelled phasor diagram to show the relationship between the generated e.m.f., the terminal voltage and the load current. (6)
- (ii) Calculate the voltage regulation. (6)
8. (a) Referring to Fig Q8, which shows the cage rotor for a three-phase, 6 pole, 60 Hz induction motor:
- (i) explain how torque is produced; (5)
- (ii) state the direction of rotation of the rotor; (1)
- (iii) explain why the rotor does not rotate at synchronous speed. (2)
- (b) Sketch and label a torque/speed characteristic for the motor, and indicate EACH of the following: (5)
- synchronous speed;
 - pull-out torque;
 - starting torque.
- (c) Calculate the rotor speed if the slip is 4%. (3)

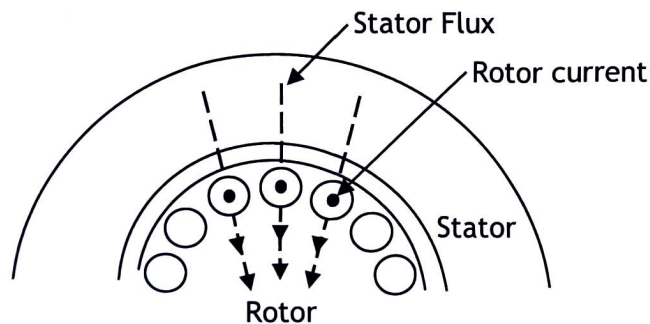


Fig Q8

9. (a) Sketch a labelled circuit diagram for a full wave three-phase rectifier supplying a load resistor. Indicate the polarity of the load terminals. (5)
- (b) For the circuit sketched in Q9(a):
- (i) summarise the circuit operation; (2)
 - (ii) state the diode conduction sequence for one cycle of the supply; (3)
 - (iii) sketch the output voltage waveform and indicate the average voltage; (3)
 - (iv) explain why a smaller value of capacitor is required to achieve the same peak-peak ripple compared to the value required for a single-phase, full wave rectifier, assuming the same supply frequency. (3)