

# ELECTROTECHNOLOGY

Attempt SIX questions only.

All questions carry equal marks.

Marks for each part question are shown in brackets.

- 0 (a) Fig Q1 represents a 230 V, 2-core RADIAL distributor with three loads. The go + return resistances for each cable section are shown.

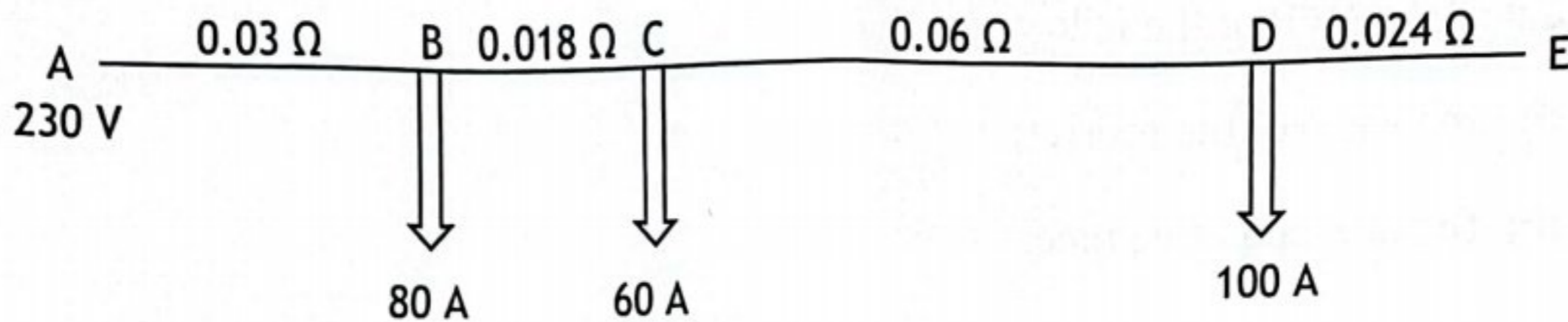


Fig Q1

Calculate EACH of the following:

- (i) the load voltage at D; (5)
  - (ii) the total power loss in the distributor. (2)
- (b) Points A and E of the distributor in Fig Q1 are connected to create a RING distributor supplied at 230 V.

Calculate EACH of the following:

- (i) the load voltage at D; (6)
- (ii) the total power dissipated in the distributor. (3)

2. A relay coil has a resistance of  $350 \Omega$  and operates when the coil current is  $80 \text{ mA}$ . When the coil is connected to a  $30 \text{ V d.c.}$  supply the relay takes  $25 \text{ ms}$  to operate.

(a) Calculate EACH of the following for the relay coil:

(i) the final value of current; (2)

(ii) the time constant; (4)

(iii) the inductance. (2)

(b) A resistor is connected in series with the relay coil and the final value of current is now  $73.89 \text{ mA}$ .

Calculate EACH of the following:

(i) the value of the resistor; (4)

(ii) the new operating time. (4)

3. Three identical coils are connected in star to a three-phase,  $440 \text{ V}$ ,  $60 \text{ Hz}$  power supply and consume a total power of  $5 \text{ kW}$  at  $0.7$  power factor lag.

Calculate EACH of the following:

(a) the resistance and reactance of each coil; (6)

(b) the total reactive power; (2)

(c) the current in EACH line if one coil is:

(i) short circuited; (5)

(ii) open circuited. (3)

4. Fig Q4 shows phasor diagrams for a 440 V, 60 Hz, 10 pole, three-phase synchronous motor with constant load when the excitation is increased:

[1] original excitation

[2] excitation is increased and the generated e.m.f. increases from  $E_1$  to  $E_2$

[3] final condition

(a) Explain EACH of the following:

(i) why the armature current  $I_A$  lags the resultant e.m.f.  $E_R$  by almost  $90^\circ$ ; (2)

(ii) why the load angle  $\delta$  reduces from  $40^\circ$  to  $35^\circ$ . (4)

(b) Calculate EACH of the following:

(i) the shaft speed; (2)

(ii) the original and the final power factor; (2)

(iii) the motor input power if  $I_{A3}$  is 150 A; (3)

(iv) the synchronous reactance per phase if  $E_{R3}$  is 159 V. (3)

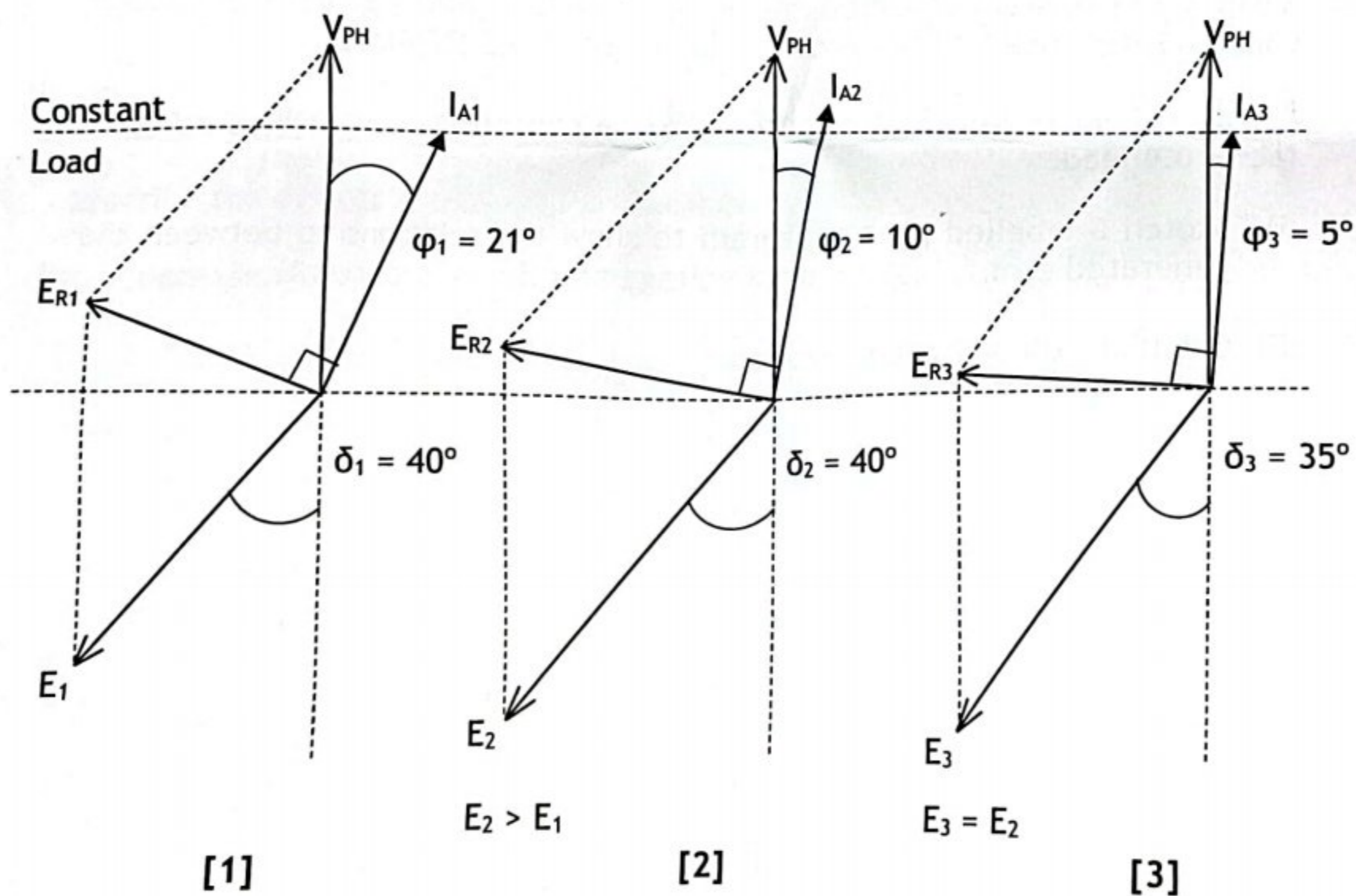


Fig Q4

[OVER

5. (a) Sketch a labelled circuit diagram for a 440 V, step-down, star connected, three-phase autotransformer with 50%, 60% and 85% tapplings. Indicate primary and secondary phase turns, voltages and currents. (5)
- (b) State TWO advantages and the main disadvantage of an autotransformer compared to a double wound transformer. (3)
- (c) A three-phase induction motor is connected to the 60% tapplings of the autotransformer in Q5(a). The motor line voltage is 264 V and the starting current is 288 A.

Calculate EACH of the following at start:

- (i) the supply line voltage; (3)
- (ii) the supply current; (3)
- (iii) the current in the common section of each transformer coil. (2)

6.

- (a) With the aid of a labelled sketch, describe the construction of a synchronous generator cylindrical rotor having two poles and slip rings. (6)
- (b) A three-phase, star connected, 500 kVA, 440 V generator has negligible stator winding resistance and synchronous reactance of  $0.3 \Omega/\text{phase}$ .

The generator is tested at rated kVA with a capacitive load having a power factor 0.9 lead.

- (i) Sketch a labelled phasor diagram to show the relationship between the generated e.m.f., the terminal voltage and the load current. (4)
- (ii) Calculate the voltage regulation. (6)

7. (a) Sketch and label a circuit diagram showing an ammeter, a voltmeter and a wattmeter fed from three-phase high voltage busbars using instrument transformers. Include the instrument transformer terminal markings. (7)
- (b) State THREE reasons why instrument transformers are used to connect the instruments in the circuit of Q7(a). (3)
- (c) The voltmeter and wattmeter monitoring the three-phase supply in Q7(a) read 11 kV and 8 MW respectively. The load power factor is 0.84 lag, the current transformer ratio is 300:1 and the voltage transformer ratio is 100:1.

Calculate EACH of the following:

- (i) the ammeter reading; (2)
- (ii) the current in the wattmeter current coil; (2)
- (iii) the voltage across the wattmeter voltage coil. (2)

8. (a) With reference to synchronising an incoming three-phase generator with an existing generator having the same phase sequence, state the control adjustments required to achieve the correct voltage, frequency and phase. (2)
- (b) Two three-phase generators having identical AVR and governor characteristics operate in parallel.

Describe the effects resulting from EACH of the following:

- (i) increase the excitation of ONE generator; (7)
- (ii) reduce the fuel supply to the prime mover of ONE generator. (7)

[OVER